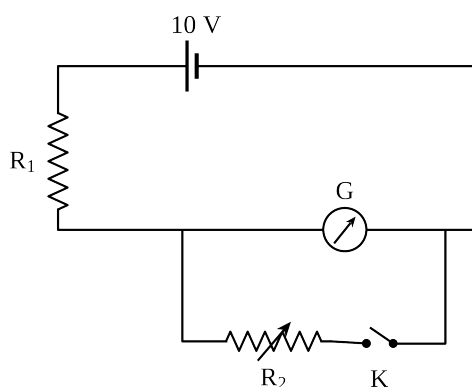


PART 1 - PHYSICS**Topic :** Experimental skills (physics)**SECTION-1 : (Maximum Marks : 4)**

- This section contains **ONE** question.
- The answer to each question is a **NUMERICAL VALUE**.
- For each question, enter the correct numerical value of the answer (in decimal notation, truncated / rounded-off to the **SECOND DECIMAL PLACE**; e.g. 6.25, 7.00, -0.33, -0.30, 30.27, -127.30) in the place designated to enter the answer.
- Answer to each question will be evaluated according to the following marking scheme :
Full Marks : +4 If ONLY the correct answer is entered;
Zero Marks : 0 In all other cases.

1. As shown in the figure, the resistance of a galvanometer G can be found by the half-deflection method. Here the resistance R_2 is adjusted such that when the key K is closed the deflection in the galvanometer becomes half of the value as compared to when K is open. Half-deflection is obtained at $R_2 = 4\ \Omega$ and thus the galvanometer resistance is found to be $6\ \Omega$. In this half-deflection condition the current (in mA) through the resistor R_1 is:

[JEE Advanced 2026 Paper 2]



Scan or tap for the full solution

**Space for Rough Work**

JEE ADVANCED EXPERIMENTAL SKILLS (PHYSICS) — GALVANOMETER: RESISTANCE AND FIGURE OF MERIT — PYQS

Test Pattern : JEE (Advanced)

ANSWER KEY

SECTION-1

Ques.	1												
Ans.	690 to 710												